

- The material used in this presentation i.e. pictures/graphs/text, etc. is solely intended for educational/teaching purpose, offered free of cost to the students for use under special circumstances of Online Education due to COVID-19 Lockdown situation and may include copyrighted material - the use of which may not have been specifically authorised by Copyright Owners. It's application constitutes Fair Use of any such copyrighted material as provided in globally accepted law of many countries. The contents of presentations are intended only for the attendees of the class being conducted by the presenter.


# Chapter 12

## Summary

### Capacitor types
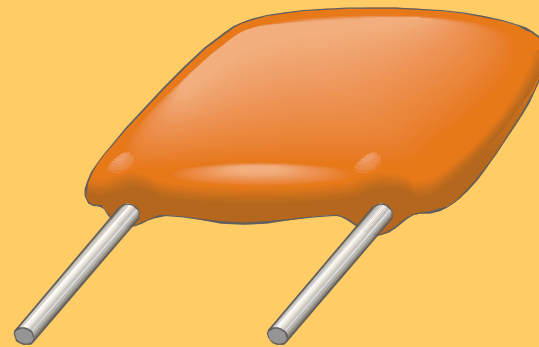
#### Mica

Mica capacitors are small with high working voltage. The **working voltage** is the voltage limit that cannot be exceeded.




# Chapter 12

## Summary

### Capacitor types
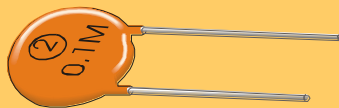
#### Ceramic disk

Ceramic disks are small nonpolarized capacitors. They have relatively high capacitance due to high  $\epsilon_r$ .



# Chapter 12

## Summary

### Capacitor types

#### Plastic Film

Plastic film capacitors are small and nonpolarized. They have relatively high capacitance due to larger plate area.




# Chapter 12

## Summary

### Capacitor types
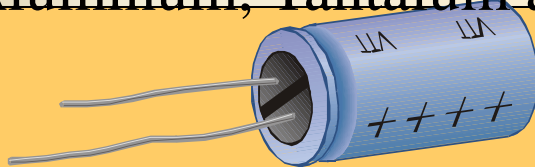
#### **Electrolytic** (two types)


Electrolytic capacitors have very high capacitance but they are not as precise as other types and tend to have more leakage current. Electrolytic types are polarized. Aluminum, Tantalum are used as electrodes or plates



Al electrolytic



Symbol for any electrolytic capacitor

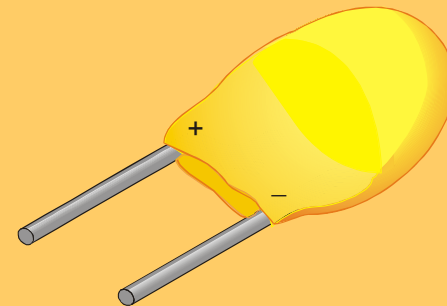

Ta electrolytic




# Chapter 12

## Summary

### Capacitor types
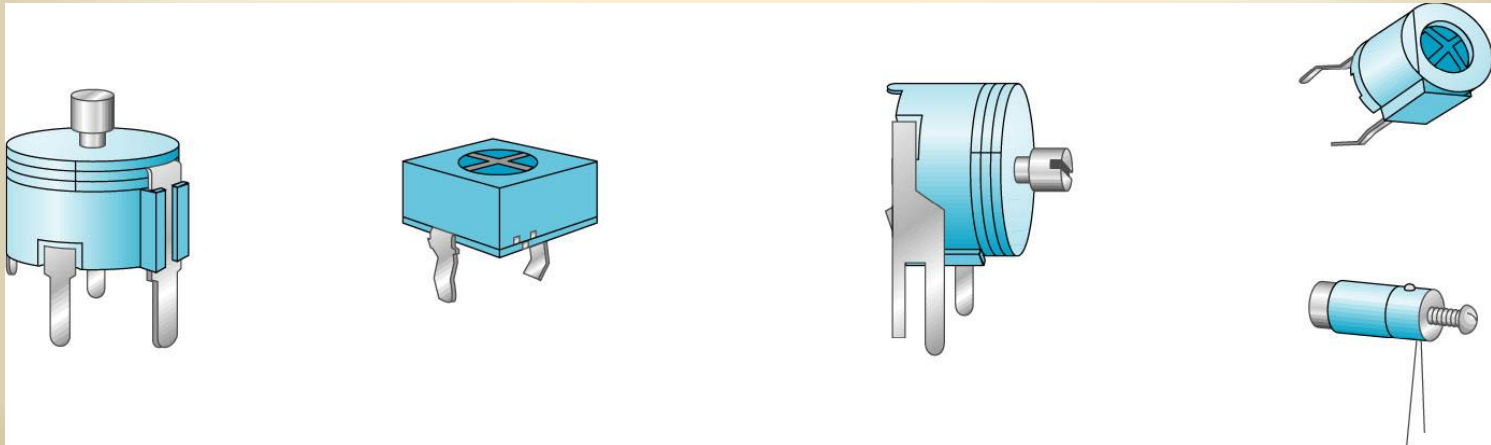
#### Variable

Variable capacitors typically have small capacitance values and are usually adjusted manually.




# Chapter 12
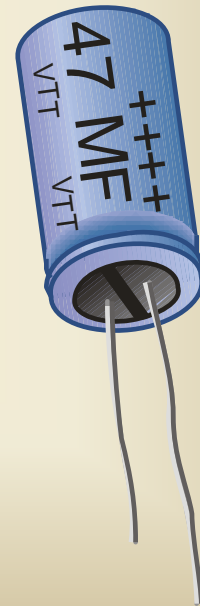
## Capacitor labeling

Capacitors use several labeling methods. Small capacitors values are frequently stamped on them such as .001 or .01, which have units of microfarads.

Electrolytic capacitors have larger values, so are read as  $\mu\text{F}$ . The unit is usually stamped as  $\mu\text{F}$ ).





# Chapter 12


## Summary
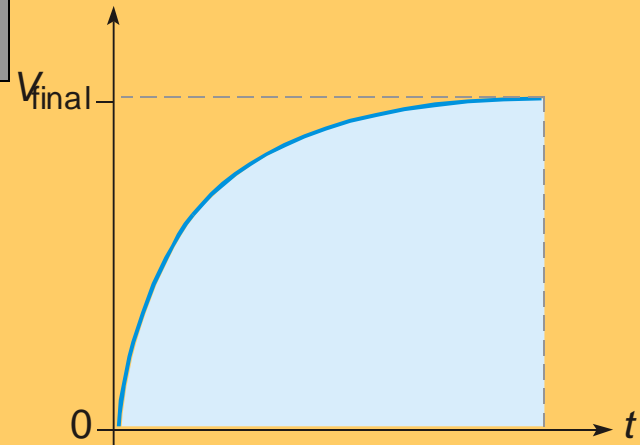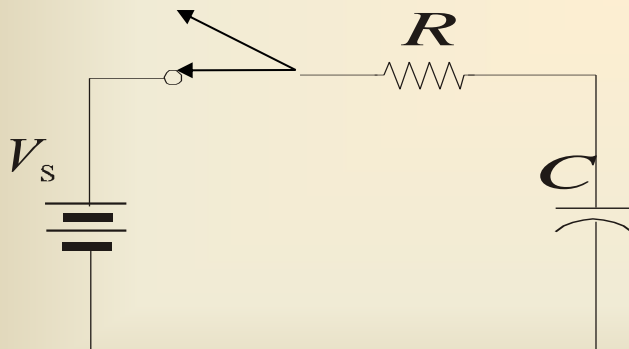
### Capacitors in dc circuits

When a capacitor is charged through a series resistor and dc source, the charging curve is exponential.



(a) Capacitor charging voltage

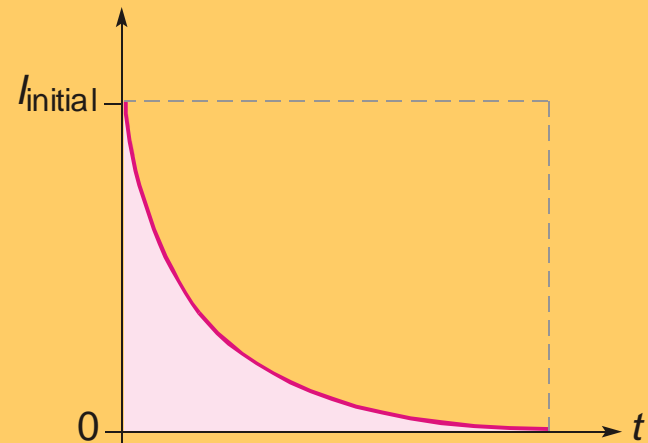

(b) Charging current





# Chapter 12


## Summary
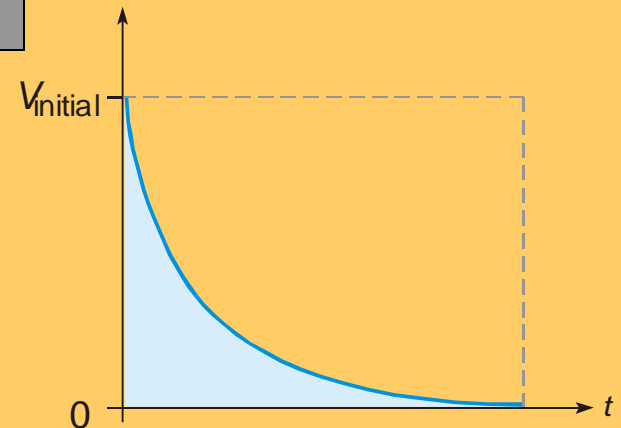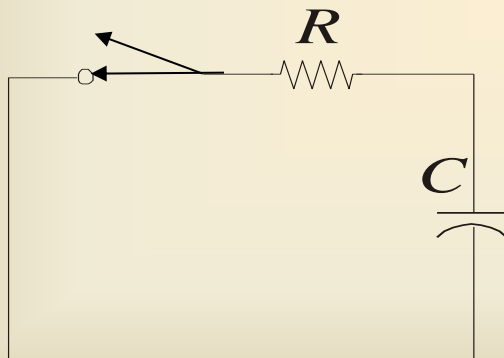
### Capacitors in dc circuits

When a capacitor is discharged through a resistor, the discharge curve is also an exponential. (Note that the current is negative.)



(a) Capacitor discharging voltage

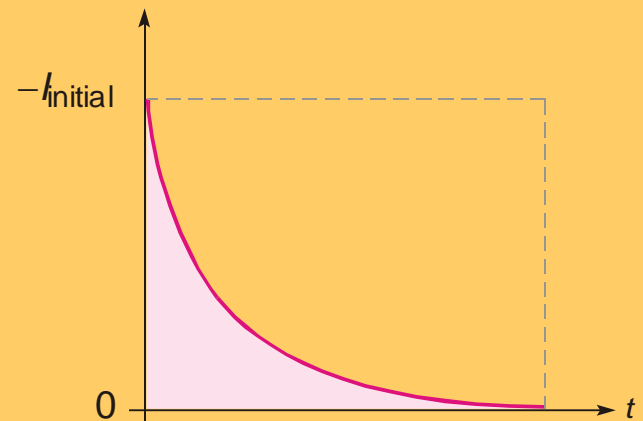

(b) Discharging current


# Chapter 12

## Summary

### Universal exponential curves

Specific values for current and voltage can be read from a universal curve. For an  $RC$  circuit, the time constant is

$$\tau = RC$$

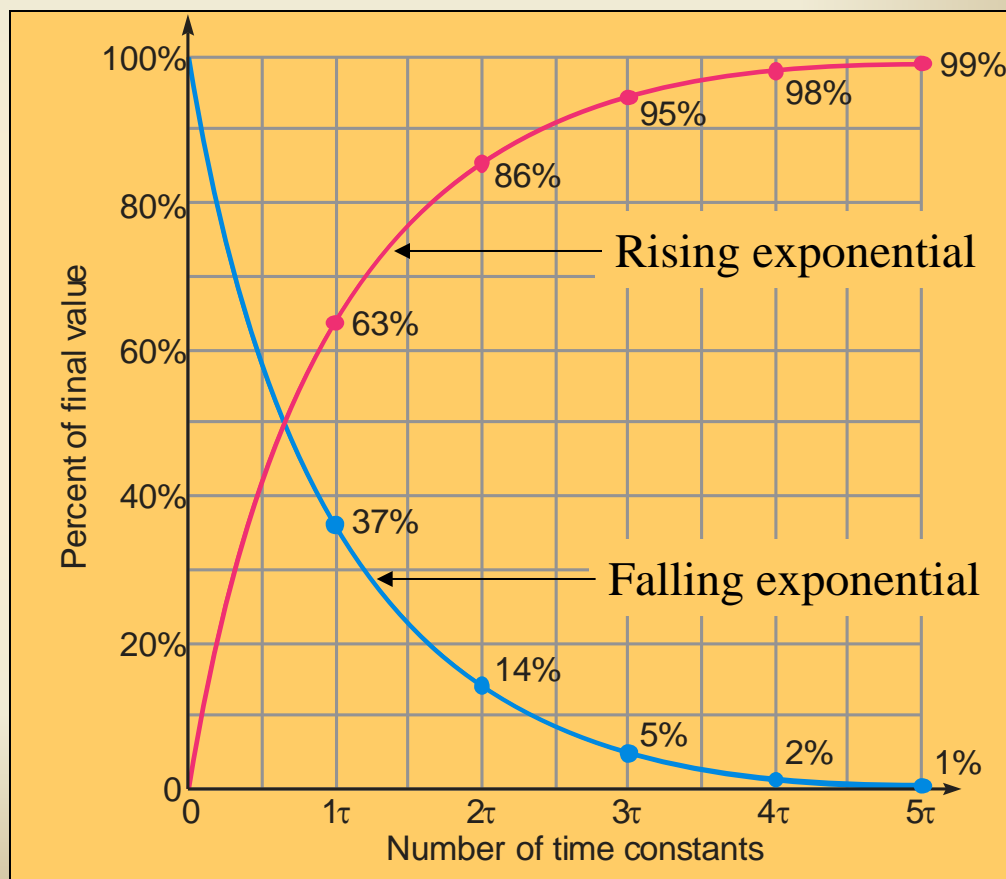

# Chapter 12

## Summary

### Capacitive reactance

**Capacitive reactance** is the opposition to ac by a capacitor. The equation for capacitive reactance is

$$X_c = \frac{1}{2\pi fC}$$

### Example


The reactance of a 0.047  $\mu\text{F}$  capacitor when a frequency of 15 kHz is applied is **226  $\Omega$**

# Chapter 12

## Summary
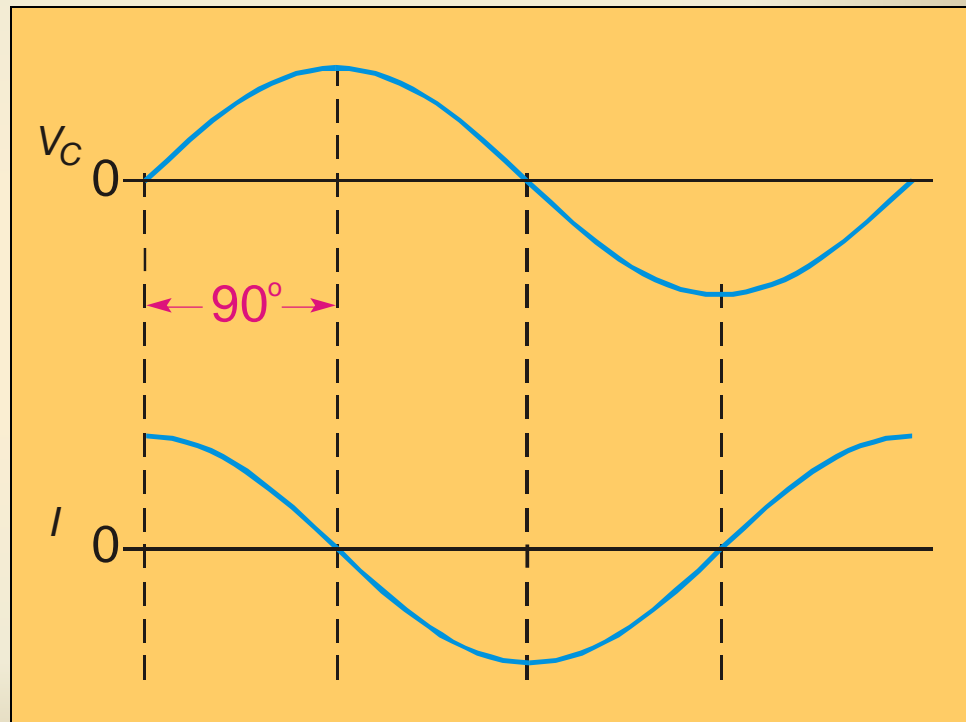
### Capacitive phase shift

When a sine wave is applied to a capacitor, there is a phase shift between voltage and current such that current always leads the voltage by  $90^\circ$ .



## Chapter 12

*Thank  
you*

